
7. An electronics hobbyist is building a radio which requires 150 Ω in her circuit. But she has only 220 Ω, 79 Ω and 92 Ω resistors available. How can she connect the available resistors to get the desired value of resistance?

Ans: Parallel combination of 220 Ω and 79 Ω in series with 92 Ω

8. A cell supplies a current of 0.9 A through a 2 Ω resistor and a current of 0.3 A through a 7 Ω resistor. Calculate the internal resistance of the cell.

Ans: 0.5 Ω

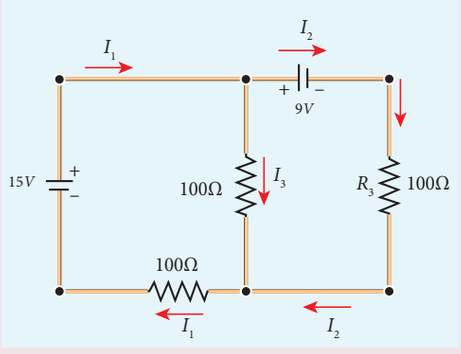9. Calculate the currents in the following circuit.




Ans : I_1 = 0.070 A, I_2 = -0.010 A and I_3 = 0.080 A

10. A potentiometer wire has a length of 4 m and resistance of 20 Ω. It is connected in series with resistance of 2980 Ω and a cell of emf 4 V. Calculate the potential gradient along the wire.

Ans: Potential = 0.65×10^{-2} V m^{-1}.

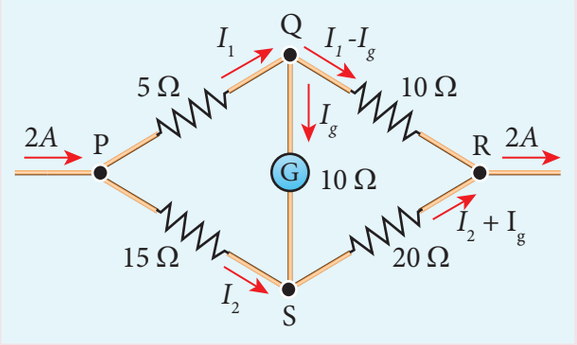11. Determine the current flowing through the galvanometer (G) as shown in the figure.



Ans: $I_g = \frac{1}{11}$ A

12. Two cells each of 5V are connected in series with a 8 Ω resistor and three parallel resistors of 4 Ω, 6 Ω and 12 Ω. Draw a circuit diagram for the above arrangement. Calculate i) the current drawn from the cells (ii) current through each resistor

Ans:

i) Current through 8 Ω = 1A

ii) The current through 4 Ω, $I = \frac{2}{4} = 0.5\text{A}$,

the current through 6 Ω, $I = \frac{2}{6} = 0.33\text{A}$,

the current through 12 Ω, $I = \frac{2}{12} = 0.17\text{A}$

13. Four bulbs P, Q, R, S are connected in a circuit of unknown arrangement. When each bulb is removed one at a time and replaced, the following behavior is observed.

	P	Q	R	S
P removed	*	on	on	on
Q removed	on	*	on	off
R removed	off	off	*	off
S removed	on	off	on	*

Draw the circuit diagram for these bulbs.

UNIT-2(XII-Physics_Vol-1).indd 122 14-02-2020 19:37:32