Note

But in practice, the Joule heating and radiation of electromagnetic waves from the circuit decrease the energy of the system. Therefore, the oscillations become damped oscillations.

4.9.2 Conservation of energy in LC oscillations

During LC oscillations in LC circuits, the energy of the system oscillates between the electric field of the capacitor and the magnetic field of the inductor. Although, these two forms of energy vary with time, the total energy remains constant. It means that LC oscillations take place in accordance with the law of conservation of energy.

$$\text{Total energy, } U = U_E + U_B = \frac{q^2}{2C} + \frac{1}{2}Li^2$$

Let us consider 3 different stages of LC oscillations and calculate the total energy of the system.

Case (i) When the charge in the capacitor, $q = Q_m$ and the current through the inductor, $i = 0$, the total energy is given by

$$U = \frac{Q_m^2}{2C} + 0 = \frac{Q_m^2}{2C} \qquad (4.56)$$

The total energy is wholly electrical.

Case (ii) When charge = 0 ; current = I_m, the total energy is

$$U = 0 + \frac{1}{2}LI_m^2 = \frac{1}{2}LI_m^2$$

$$= \frac{L}{2} \times \left(\frac{Q_m^2}{LC}\right) \quad \text{since } I_m = Q_m\omega = \frac{Q_m}{\sqrt{LC}}$$

$$= \frac{Q_m^2}{2C} \qquad (4.57)$$

The total energy is wholly magnetic.

Case (iii) When charge = q; current = i, the total energy is

$$U = \frac{q^2}{2C} + \frac{1}{2}Li^2$$

Since $q = Q_m \cos\omega t$, $i = -\frac{dq}{dt} = Q_m\omega \sin\omega t$. The negative sign in current indicates that the charge in the capacitor decreases with time.

$$U = \frac{Q_m^2 \cos^2\omega t}{2C} + \frac{L\omega^2 Q_m^2 \sin^2\omega t}{2}$$

$$= \frac{Q_m^2 \cos^2\omega t}{2C} + \frac{LQ_m^2 \sin^2\omega t}{2LC}$$

$$\text{since } \omega^2 = \frac{1}{LC}$$

$$= \frac{Q_m^2}{2C}\left(\cos^2\omega t + \sin^2\omega t\right)$$

$$U = \frac{Q_m^2}{2C} \qquad (4.58)$$

From above three cases, it is clear that the total energy of the system remains constant.

4.9.3 Analogies between LC oscillations and simple harmonic oscillations

Qualitative treatment

The electromagnetic oscillations of LC system can be compared with the mechanical oscillations of a spring-mass system.

There are two forms of energy involved in LC oscillations. One is electrical energy of the charged capacitor; the other magnetic energy of the inductor carrying current.

UNIT-4(XII-Physics_Vol-1).indd 253 17-02-2020 13:20:16