6. A circular coil with a cross-sectional area of 4 cm^2 has 10 turns. It is placed at the centre of a long solenoid that has 15 turns/cm and a cross-sectional area of 10 cm^2. The axis of the coil coincides with the axis of the solenoid. What is their mutual inductance?

(a) 7.54 μH (b) 8.54 μH

(c) 9.54 μH (d) 10.54 μH

7. In a transformer, the number of turns in the primary and the secondary are 410 and 1230 respectively. If the current in primary is 6A, then that in the secondary coil is

(a) 2 A (b) 18 A

(c) 12 A (d) 1 A

8. A step-down transformer reduces the supply voltage from 220 V to 11 V and increase the current from 6 A to 100 A. Then its efficiency is

(a) 1.2 (b) 0.83

(c) 0.12 (d) 0.9

9. In an electrical circuit, *R, L, C* and AC voltage source are all connected in series. When *L* is removed from the circuit, the phase difference between the voltage and current in the circuit is $\pi/3$. Instead, if C is removed from the circuit, the phase difference is again $\pi/3$. The power factor of the circuit is

(NEET 2012)

(a) $1/2$ (b) $1/\sqrt{2}$

(c) 1 (d) $\sqrt{3}/2$

10. In a series RL circuit, the resistance and inductive reactance are the same. Then the phase difference between the voltage and current in the circuit is

(a) $\frac{\pi}{4}$ (b) $\frac{\pi}{2}$

(c) $\frac{\pi}{6}$ (d) zero

11. In a series resonant *RLC* circuit, the voltage across 100 Ω resistor is 40 V. The resonant frequency ω is 250 rad/s. If the value of C is 4 μF, then the voltage across L is

(a) 600 V (b) 4000 V

(c) 400V (d) 1 V

12. An inductor 20 mH, a capacitor 50 μF and a resistor 40 Ω are connected in series across a source of emf V = 10 sin 340 t. The power loss in AC circuit is

(a) 0.76 W (b) 0.89 W

(c) 0.46 W (d) 0.67 W

13. The instantaneous values of alternating current and voltage in a circuit are

$i = \frac{1}{\sqrt{2}}\sin(100\pi t)$ A and

$v = \frac{1}{\sqrt{2}}\sin\left(100\pi t + \frac{\pi}{3}\right)$ V.

The average power in watts consumed in the circuit is (IIT Main 2012)

(a) $\frac{1}{4}$ (b) $\frac{\sqrt{3}}{4}$

(c) $\frac{1}{2}$ (d) $\frac{1}{8}$

14. In an oscillating LC circuit, the maximum charge on the capacitor is Q. The charge on the capacitor when the energy is stored equally between the electric and magnetic fields is

(a) $\frac{Q}{2}$ (b) $\frac{Q}{\sqrt{3}}$

(c) $\frac{Q}{\sqrt{2}}$ (d) Q

UNIT-4(XII-Physics_Vol-1).indd 259 17-02-2020 13:20:35