## OBSERVATION

Table: To find the ratio of emf of two cells

| S.No | Balancing length for Lechlanche cell, $l_1$ (cm) | Balancing length for Daniel cell, $l_2$ (cm) | $\frac{\varepsilon_1}{\varepsilon_2} = \frac{l_1}{l_2}$ |
|---|---|---|---|
| 1 | | | |
| 2 | | | |
| 3 | | | |
| 4 | | | |
| 5 | | | |

Mean $\frac{\varepsilon_1}{\varepsilon_2} =$

## CALCULATION

$$\frac{\varepsilon_1}{\varepsilon_2} = \frac{l_1}{l_2}$$

## RESULT

Ratio of emf of the given two cells = _____ (no unit)

**Note:**

**DPDT switch**



Double Pole Double Throw (DPDT) switch is a 6-terminal key with a throw switch (metal handle) attached to the common terminals M and N. The two-given cells are connected to the pairs of terminals $M_1$ & $M_2$ and
$N_1$ & $N_2$. When the handle is thrown to one side, say $M_1$ & $M_2$, the cell that is connected to that pair of terminals is included with the primary circuit.



XII-Physics_Vol-1) PRACTICAL.indd 295 14-02-2020 20:12:58