
(ii) Output characteristic curve: V_{CE} vs I_C (I_B constant)

- The base current I_B is kept constant.
- V_{CE} is varied in steps of 1V and the corresponding collector current I_C is noted. The readings are taken till the collector current becomes almost constant.
- Initially I_B is kept at 0 mA and the corresponding collector current is noted. This current is the reverse saturation current I_{CEO}.
- The experiment is repeated for various values of I_B. The readings are tabulated.
- A graph is drawn by taking V_{CE} along x-axis and I_C along y-axis for various values of I_B.
- The set of curves thus obtained is called the output characteristics of a transistor.
- The reciprocal of the slope of the curve gives output impedance of the transistor.

S. No	I_B =20 μA		I_B =40 μA	
	V_{CE} (V)	I_C (mA)	V_{CE} (V)	I_C (mA)

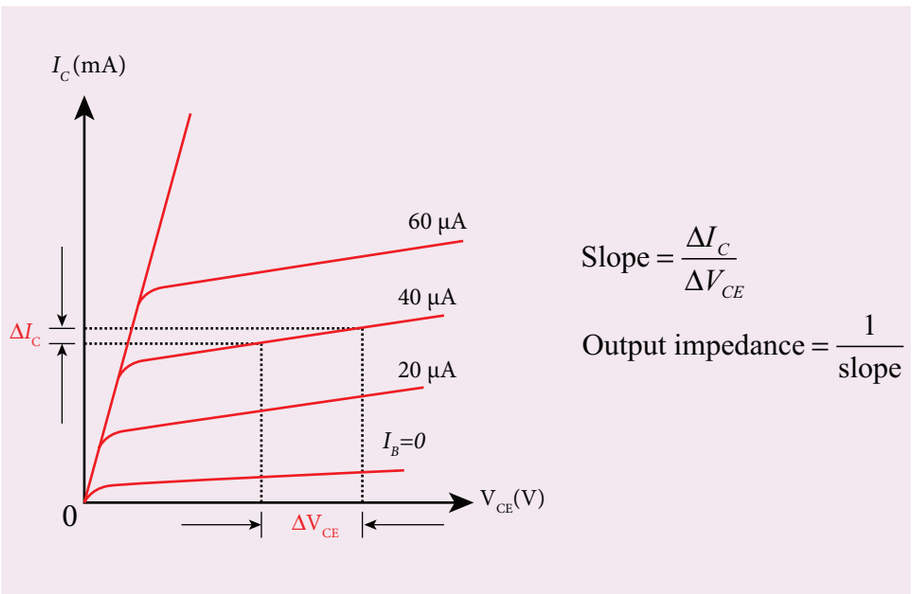

$$\text{Slope} = \frac{\Delta I_C}{\Delta V_{CE}}$$

$$\text{Output impedance} = \frac{1}{\text{slope}}$$

(iii) Transfer characteristic curve: I_B vs I_C (V_{CE} constant)

- The collector-emitter voltage V_{CE} is kept constant.
- The base current I_B is varied in steps of 10 μA and the corresponding collector current I_C is noted.
- This is repeated by changing the value of V_{CE}. The readings are tabulated.
- The transfer characteristics is a plot between the input current IB along x-axis and the output current I_C along y-axis keeping V_{CE} constant.
- The slope of the transfer characteristics plot gives the current gain β can be calculated.

XII-Physics_Vol-1) PRACTICAL.indd 312 14-02-2020 20:13:07