10. VERIFICATION OF DE MORGAN'S THEOREMS

AIM: To verify De Morgan's first and second theorems.

COMPONENTS REQUIRED: Power Supply (0 – 5V), IC 7400, 7408, 7432, 7404, and 7402, Digital IC trainer kit, connecting wires.


FORMULA

De Morgan's first theorem $\overline{A+B} = \overline{A}.\overline{B}$


De Morgan's second theorem $\overline{A.B} = \overline{A}+\overline{B}$

CIRCUIT DIAGRAM:

De Morgan's first theorem

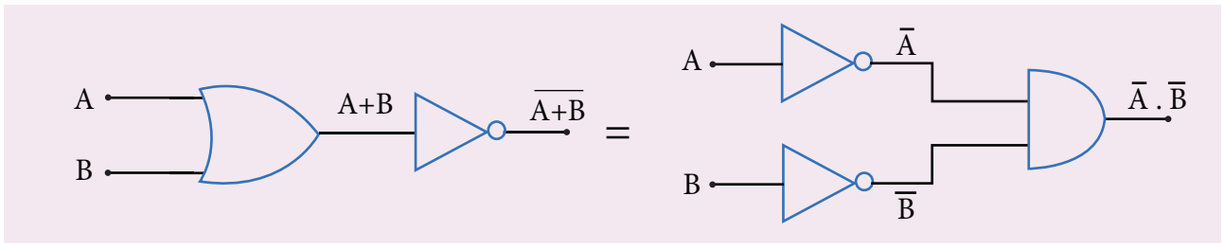

De Morgan's second theorem

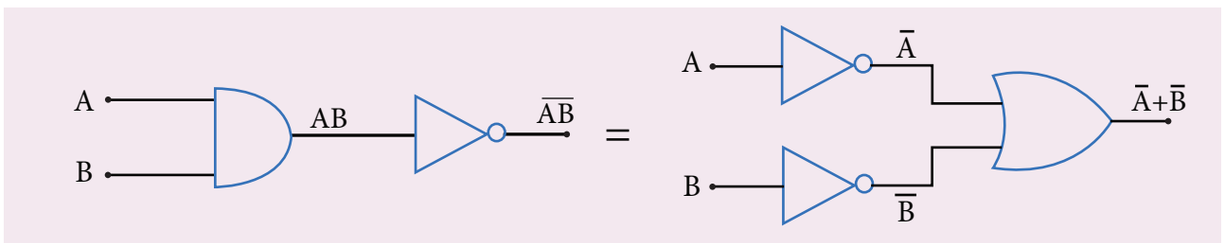

PROCEDURE:

i) Verification of De Morgan's first theorem

- The connections are made for LHS $\left[\overline{A+B}\right]$ of the theorem as shown in the circuit diagram using appropriate ICs.
- The output is noted and tabulated for all combinations of logical inputs of the truth table.
- The same procedure is repeated for RHS $\left[\overline{A}.\overline{B}\right]$ of the theorem.
- From the truth table, it can be shown that $\overline{A+B} = \overline{A}.\overline{B}$.

XII-Physics_Vol-1) PRACTICAL.indd 316 14-02-2020 20:13:11