Solution

Since the resistors are connected in series, the effective resistance in the circuit

$= 4\ \Omega + 6\ \Omega = 10\ \Omega$

current I in the circuit $= \frac{V}{R_{eq}} = \frac{24}{10} = 2.4\,\text{A}$

Voltage across 4Ω resistor

$$V_1 = IR_1 = 2.4\,\text{A} \times 4\Omega = 9.6\,\text{V}$$

Voltage across 6 Ω resistor

$$V_2 = IR_2 = 2.4\,\text{A} \times 6\Omega = 14.4\,\text{V}$$

Resistors in parallel

Resistors are in parallel when they are connected across the same potential difference as shown in Figure 2.10 (a).

In this case, the total current I that leaves the battery is split into three separate components. Let I_1, I_2 and I_3 be the current through the resistors R_1, R_2 and R_3 respectively. Due to the conservation of charge, total current in the circuit I is equal to sum of the currents through each of the three resistors.

$$I = I_1 + I_2 + I_3 \qquad (2.24)$$

Since the voltage across each resistor is the same, applying Ohm's law to each resistor, we have

$$I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}, I_3 = \frac{V}{R_3} \qquad (2.25)$$

Substituting these values in equation (2.24),we get

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V\left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right]$$

$$I = \frac{V}{R_P}$$

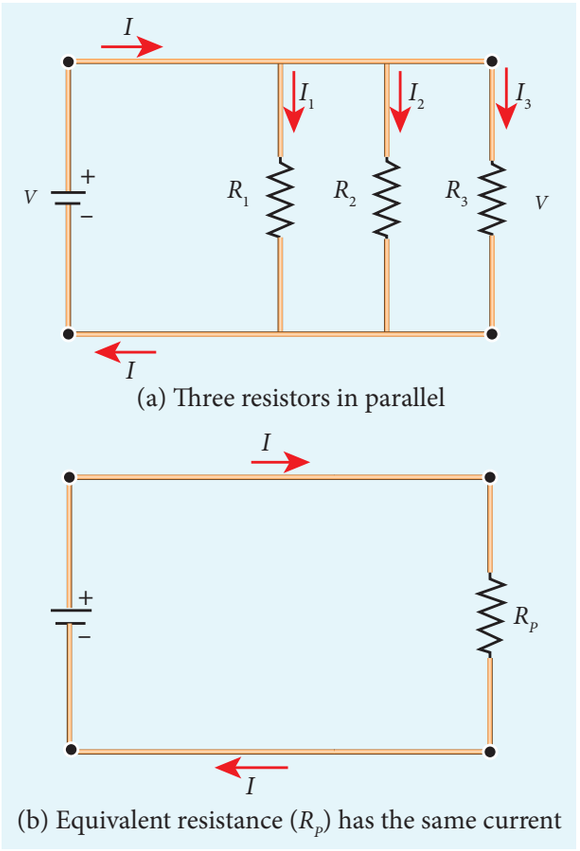


Figure 2.10 Resistors in parallel

$$\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \qquad (2.26)$$

Here R_P is the equivalent resistance of the parallel combination of the resistors. Thus, when a number of resistors are connected in parallel, the sum of the reciprocals of resistance of the individual resistors is equal to the reciprocal of the effective resistance of the combination as shown in the Figure 2.10 (b).

Note: The value of equivalent resistance in parallel connection will be lesser than each individual resistance.

House hold appliances are always connected in parallel so that even if one is switched off, the other devices could function properly.

UNIT-2(XII-Physics_Vol-1).indd 91 14-02-2020 19:36:56