
6. Determine the current flowing through 3Ω and 4Ω resistors of the circuit given below. Assume that diodes D_1 and D_2 are ideal diodes.

[Ans: 0 and 2A]

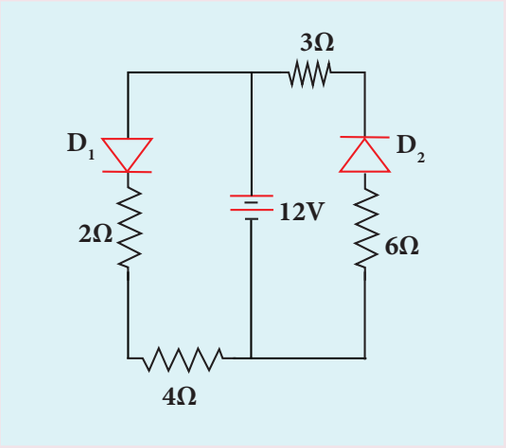

7. Prove the following Boolean expressions using the laws and theorems of Boolean algebra.

i) $(A+B)\,(A+\overline{B}) = A$


ii) $A(\overline{A}+B) = AB$

iii) $(A+B)\,(A+C) = A+BC$

8. Verify the given Boolean equation $A + \overline{A}B = A + B$ using truth table.


9. In the given figure of a voltage regulator, a Zener diode of breakdown voltage 10V is employed. Determine the current through the load resistance, the total current and the current through the diode. Use diode approximation.

[Ans: 5mA; 20 mA; 15 mA]

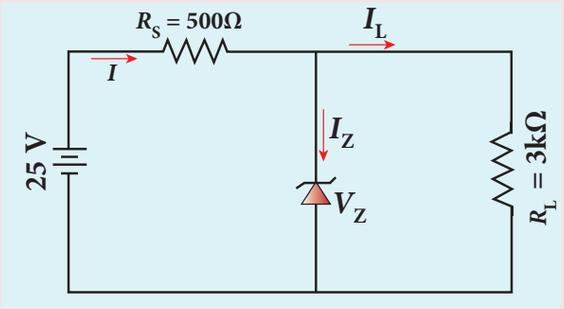

10. Write down Boolean equation for the output Y of the given circuit and give its truth table.

[Ans: $Y = (AB)+(\overline{A+B})$]

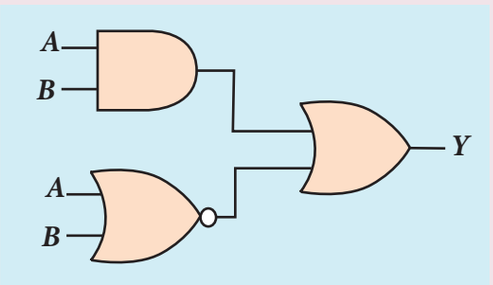

UNIT-10(XII-Physics_Vol-2)_New.indd 250 21-07-2020 15:37:30